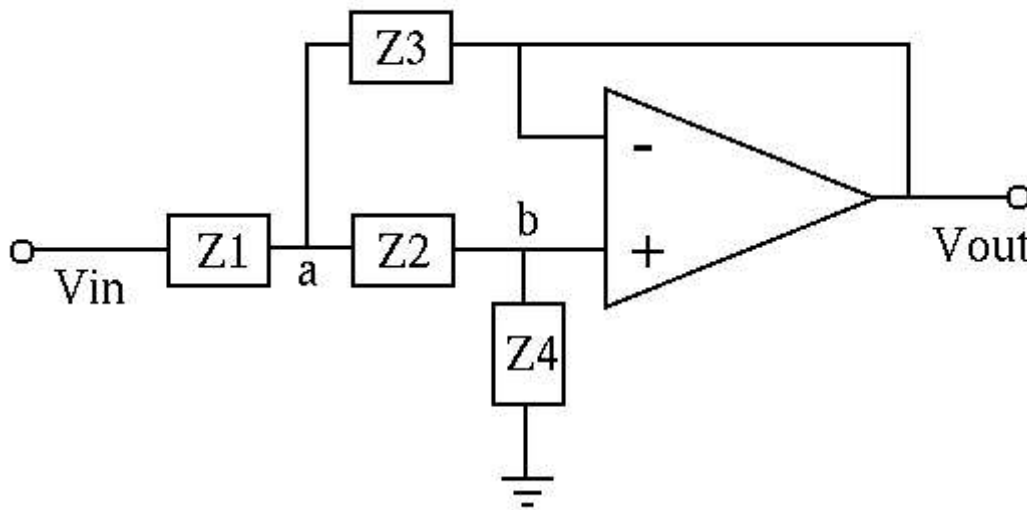




Next: [The Twin-T notch \(band-stop\)](#) **Up:** [Chapter 6: Active Filter](#) **Previous:** [First and Second Order](#)

The Sallen-Key filters

The [Sallen-Key filters](#) are second-order active filters (low-pass, high-pass, and band-pass) that can be easily implemented using the configuration below:



We represent all voltages in phasor form. Due to the virtual ground assumption, $V_b \approx V_{out}$ at non-inverting input is virtually the same as that at the inverting input, which is connected to the output V_{out} . Applying KCL to nodes a and b to get:

$$\frac{V_a - V_{in}}{Z_1} + \frac{V_a - V_{out}}{Z_3} + \frac{V_a - V_{out}}{Z_2} = \frac{V_a - V_{in}}{Z_1} + (V_a - V_{out}) \left(\frac{1}{Z_3} + \frac{1}{Z_2} \right) = 0$$

and

$$\frac{V_{out} - V_a}{Z_2} + \frac{V_{out}}{Z_4} = 0,$$

The second equation can also be written as

$$V_a - V_{out} = V_{out} \frac{Z_2}{Z_4}, \quad V_a = V_{out} \frac{Z_2 + Z_4}{Z_4}$$

Substituting these into the first equation we get

$$V_{out} \left(\frac{Z_2 + Z_4}{Z_1 Z_4} + \frac{Z_2}{Z_3 Z_4} + \frac{Z_2}{Z_2 Z_4} \right) = \frac{V_{in}}{Z_1}$$

Now the frequency response of the Sallen-Key filter can be found as the ratio of V_{out} and V_{in} :

$$H = \frac{V_{out}}{V_{in}} = \frac{Z_3 Z_4}{Z_1 Z_2 + Z_1 Z_3 + Z_2 Z_3 + Z_3 Z_4}$$

- **Second order low-pass filter**

If we let $Z_1 = R_1$, $Z_2 = R_2$, $Z_3 = 1/j\omega C_1$, $Z_4 = 1/j\omega C_2$, then the FRF becomes:

$$\begin{aligned} H(j\omega) &= \frac{1/(j\omega)^2 C_1 C_2}{R_1 R_2 + (R_1 + R_2)/j\omega C_1 + 1/(j\omega)^2 C_1 C_2} \\ &= \frac{1/R_1 R_2 C_1 C_2}{(j\omega)^2 + j\omega(R_1 + R_2)/R_1 R_2 C_1 + 1/R_1 R_2 C_1 C_2} \\ &= \frac{1/R_1 R_2 C_1 C_2}{(j\omega)^2 + j\omega/R_p C_1 + 1/R_1 R_2 C_1 C_2} \\ &= \frac{\omega_n^2}{(j\omega)^2 + 2\zeta\omega_n j\omega + \omega_n^2} = \frac{\omega_n^2}{(j\omega)^2 + \omega_n/Q j\omega + \omega_n^2} = \frac{\omega_n^2}{(j\omega)^2 + \Delta\omega j\omega + \omega_n^2} \end{aligned}$$

This is a 2nd-order low-pass filter with

$$\omega_n = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}, \quad \Delta\omega = \frac{1}{(R_1 || R_2) C_1} = \frac{1}{R_p C_1}, \quad R_p = R_1 || R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

and

$$Q = \frac{\omega_n}{\Delta\omega} = \frac{\sqrt{R_1 R_2 C_1 C_2}}{(R_1 + R_2) C_2}, \quad \zeta = \frac{1}{2Q} = \frac{(R_1 + R_2) C_2}{2\sqrt{R_1 R_2 C_1 C_2}}$$

As there are only two parameters ω_n and ζ or $Q = 1/2\zeta$ to satisfy, we can arbitrarily set any two of the four variables R_1 , R_2 , C_1 , and C_2 , and then solve for the other two. For example, for convenience, if we let $R_1 = R_2 = 1$, we get

$$\omega_n = \frac{1}{\sqrt{C_1 C_2}}, \quad \Delta\omega = \frac{1}{C_1}$$

- **Second order high-pass filter**

If we let $Z_1 = 1/j\omega C_1$, $Z_2 = 1/j\omega C_2$, $Z_3 = R_1$, $Z_4 = R_2$, then the FRF becomes:

$$\begin{aligned} H(j\omega) &= \frac{R_1 R_2}{1/(j\omega)^2 C_1 C_2 + R_1(1/j\omega C_1 + 1/j\omega C_2) + R_1 R_2} \\ &= \frac{(j\omega)^2}{1/R_1 R_2 C_1 C_2 + j\omega (C_1 + C_2)/C_1 C_2 R_2 + (j\omega)^2} \\ &= \frac{(j\omega)^2}{(j\omega)^2 + j\omega / C_s R_2 + 1/R_1 R_2 C_1 C_2} \\ &= \frac{(j\omega)^2}{(j\omega)^2 + 2\zeta\omega_n j\omega + \omega_n^2} = \frac{(j\omega)^2}{(j\omega)^2 + \omega_n/Q j\omega + \omega_n^2} = \frac{(j\omega)^2}{(j\omega)^2 + \Delta\omega j\omega + \omega_n^2} \end{aligned}$$


This is a 2nd-order high-pass filter with

$$\omega_n = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}, \quad \Delta\omega = \frac{1}{C_s R_2}, \quad C_s = \frac{C_1 C_2}{C_1 + C_2}$$

and

$$Q = \frac{\sqrt{R_1 R_2 C_1 C_2}}{(C_1 + C_2) R_1}, \quad \zeta = \frac{1}{2Q} = \frac{(C_1 + C_2) R_1}{2\sqrt{R_1 R_2 C_1 C_2}}$$

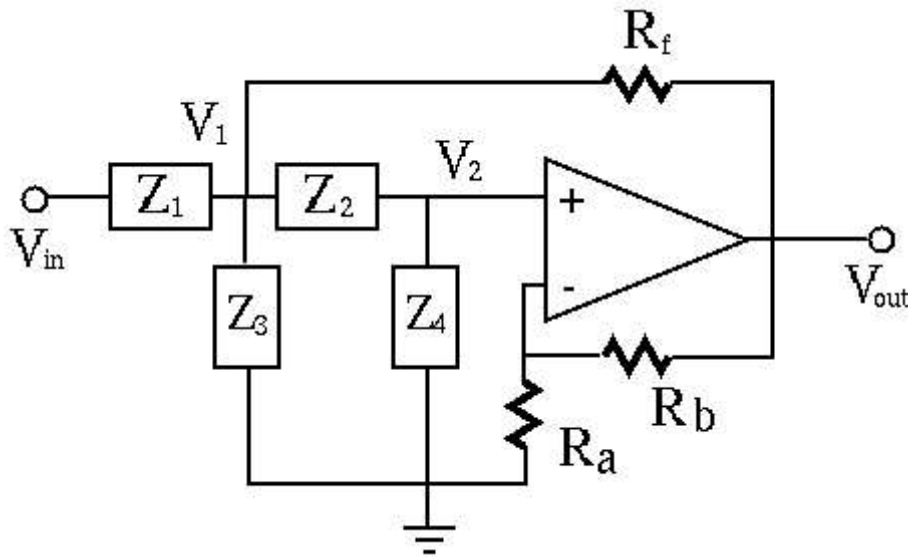We further consider a band-pass filter shown below:



By voltage divider and virtual ground, we get

$$V_2 = \frac{R_a}{R_a + R_b} V_{out} = k V_{out}, \quad \left(k = \frac{R_a}{R_a + R_b} \right)$$

Apply KCL to node V_2 to get:

$$\frac{V_1 - V_2}{Z_2} = \frac{V_2}{Z_4}, \quad \text{i.e.} \quad V_1 = V_2 \left(\frac{1}{Z_2} + \frac{1}{Z_4} \right) Z_2 = V_2 \left(1 + \frac{Z_2}{Z_4} \right)$$

Apply KCL to node V_1 to get:

$$\frac{V_{in} - V_1}{Z_1} + \frac{V_{out} - V_1}{R_f} + \frac{V_2 - V_1}{Z_2} = \frac{V_1}{Z_3}$$

Rearrange the terms, and replace V_1 by $V_2(1 + Z_2/Z_4)$ to get

$$\begin{aligned} \frac{V_{in}}{Z_1} + \frac{V_{out}}{R_f} + \frac{V_2}{Z_2} &= V_1 \left(\frac{1}{Z_1} + \frac{1}{R_f} + \frac{1}{Z_2} + \frac{1}{Z_3} \right) \\ &= V_2 \left(1 + \frac{Z_2}{Z_4} \right) \left(\frac{1}{Z_1} + \frac{1}{R_f} + \frac{1}{Z_2} + \frac{1}{Z_3} \right) \end{aligned}$$

Further rearrange the terms and replace V_2 by $k V_{out}$ to get

$$\frac{V_{in}}{Z_1} + \frac{V_{out}}{R_f} = kV_{out} \left[\left(1 + \frac{Z_2}{Z_4}\right) \left(\frac{1}{Z_1} + \frac{1}{R_f} + \frac{1}{Z_2} + \frac{1}{Z_3}\right) - \frac{1}{Z_2} \right]$$

Further rearrange the terms

$$\begin{aligned} \frac{V_{in}}{Z_1} &= kV_{out} \left[\left(1 + \frac{Z_2}{Z_4}\right) \left(\frac{1}{Z_1} + \frac{1}{R_f} + \frac{1}{Z_2} + \frac{1}{Z_3}\right) - \frac{1}{Z_2} \right] - \frac{V_{out}}{R_f} \\ &= V_{out} \left\{ k \left[\left(1 + \frac{Z_2}{Z_4}\right) \left(\frac{1}{Z_1} + \frac{1}{R_f} + \frac{1}{Z_2} + \frac{1}{Z_3}\right) - \frac{1}{Z_2} \right] - \frac{1}{R_f} \right\} \end{aligned}$$

Finally we get the frequency response function:

$$\begin{aligned} H = \frac{V_{out}}{V_{in}} &= \frac{1}{Z_1 \left\{ k \left[\left(1 + \frac{Z_2}{Z_4}\right) \left(\frac{1}{Z_1} + \frac{1}{R_f} + \frac{1}{Z_2} + \frac{1}{Z_3}\right) - \frac{1}{Z_2} \right] - \frac{1}{R_f} \right\}} \\ &= \frac{1/k}{Z_1 \left[\left(1 + \frac{Z_2}{Z_4}\right) \left(\frac{1}{Z_1} + \frac{1}{R_f} + \frac{1}{Z_2} + \frac{1}{Z_3}\right) - \frac{1}{Z_2} \right] - \frac{Z_1}{kR_f}} \\ &= \frac{1/k}{1 + \frac{Z_1}{R_f} + \frac{Z_1}{Z_3} + \frac{Z_2}{Z_4} + \frac{Z_1Z_2}{Z_4R_f} + \frac{Z_1}{Z_4} + \frac{Z_1Z_2}{Z_3Z_4} - \frac{Z_1}{kR_f}} \end{aligned}$$

If we let

$$Z_1 = R_1, \quad Z_4 = R_2, \quad Z_2 = \frac{1}{j\omega C_2}, \quad Z_3 = \frac{1}{j\omega C_1}$$

the frequency response function becomes

$$\begin{aligned} H &= \frac{\left(1 + \frac{R_b}{R_a}\right) \frac{1}{R_1 C_1} j\omega}{(j\omega)^2 + \left(\frac{1}{R_2 C_1} + \frac{1}{R_2 C_2} + \frac{1}{R_1 C_1} - \frac{R_b}{R_a R_f C_1}\right) j\omega + \frac{R_1 + R_f}{R_f R_1 R_2 C_1 C_2}} \\ &= \frac{A j\omega}{(j\omega)^2 + \Delta \omega j\omega + \omega_n^2}, \quad A = (1 + R_b/R_a)/R_1 C_1 \end{aligned}$$

This is a band-pass filter with the peak frequency equal to the natural frequency:




$$\omega_n = \sqrt{\frac{R_1 + R_f}{R_f R_1 R_2 C_1 C_2}}$$

the bandwidth

$$\Delta\omega = \frac{1}{R_2C_1} + \frac{1}{R_2C_2} + \frac{1}{R_1C_1} - \frac{R_b}{R_aR_fC_1}$$

The gain of the filter is controlled by $1 + R_b/R_a$.

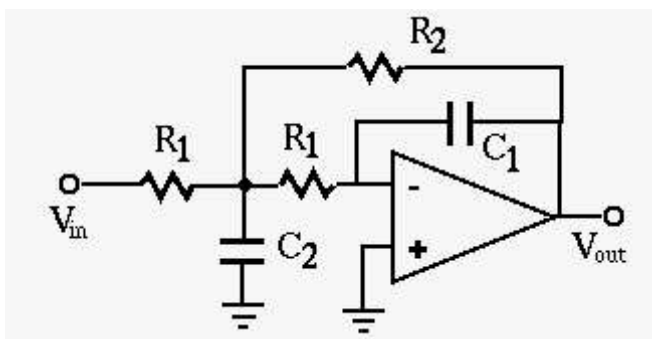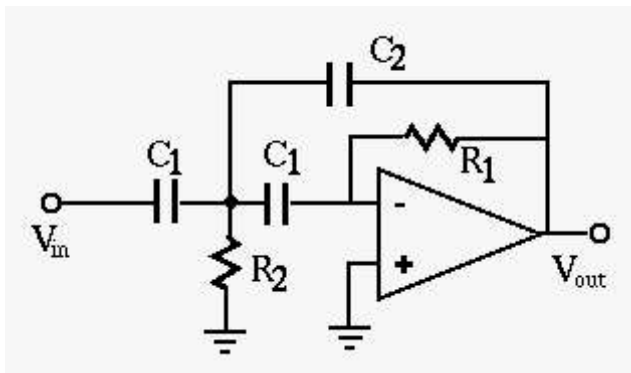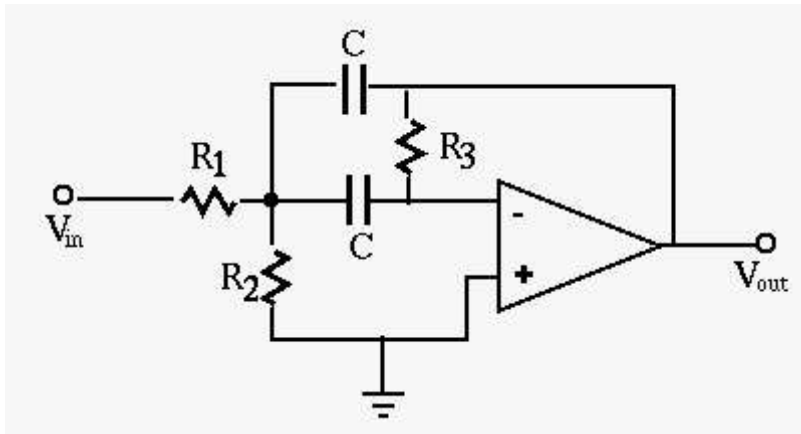More Examples of op-amp filters are listed below (with detailed analysis in [here](#)):



Next: [The Twin-T notch \(band-stop\)](#) **Up:** [Chapter 6: Active Filter](#) **Previous:** [First and Second Order](#)
 Ruye Wang 2019-05-07